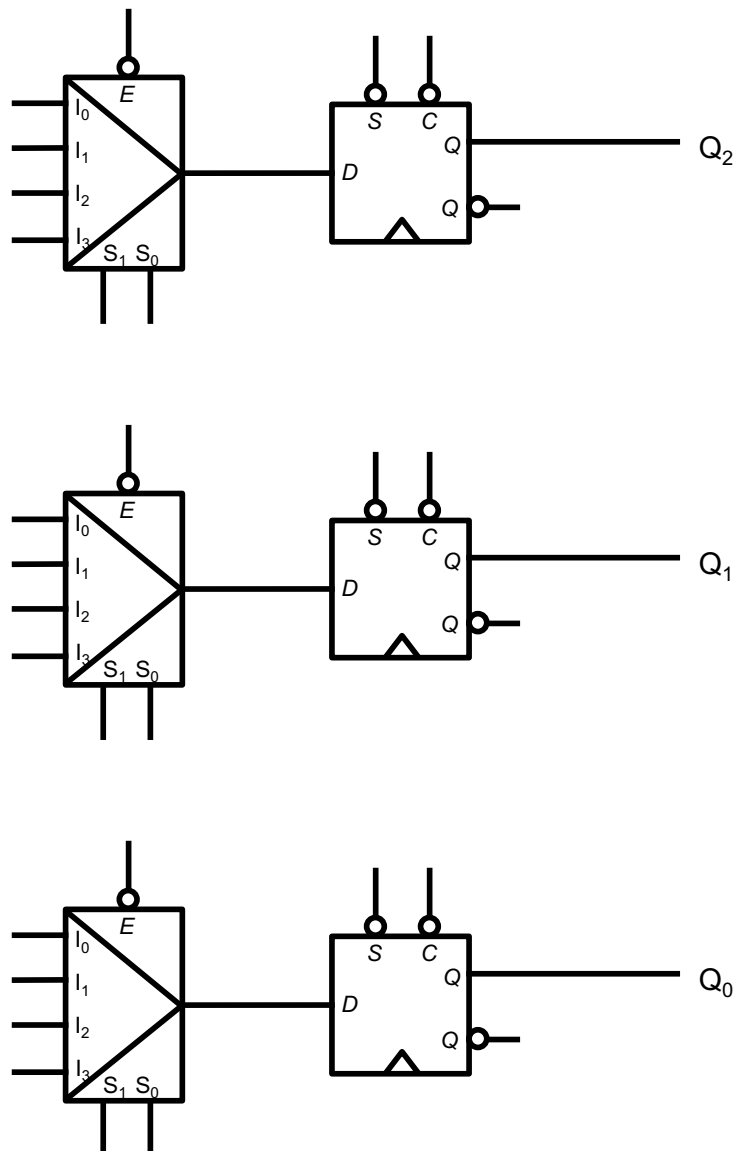




INTRODUCTION TO COMPUTERS LAB 4 NOTEBOOK

Design



Show for each element and port the chip number and corresponding pin